

3.1 **Combinational circuit synthesis tools**

Jean-Pierre Deschamps

University Rovira i Virgili, Tarragona, Spain


Design of combinational circuits: practical questions

- Redundant terms.
- Boolean function optimization tools.

1. Redundant terms (*don't care*)

Some combinations of input signal values could **never occur**, or, when they occur, the output signal values do not matter (**don't care**). The corresponding minterms can be used, or not, in order to optimize the final circuit.


EXAMPLE: BCD to 7-segment decoder.

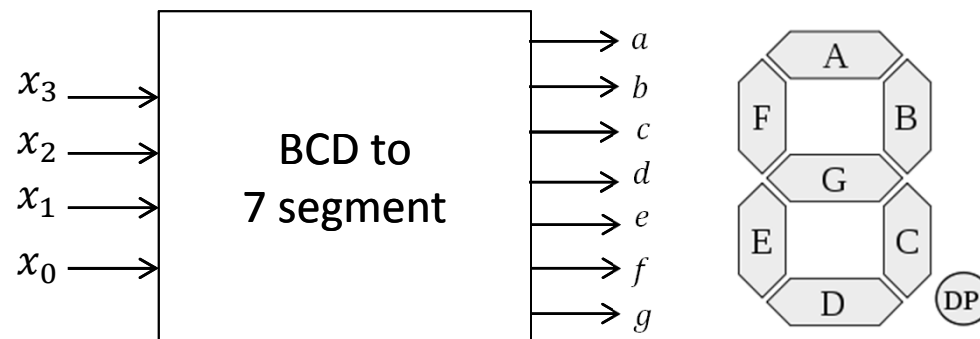

1. Redundant terms (*don't care*)

EXAMPLE: BCD to 7-segment decoder.

x3	x2	x1	x0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0							
1	0	1	1							
1	1	0	0							
1	1	0	1							
1	1	1	0							
1	1	1	1							
1	1	1	1							

 

1. Redundant terms (*don't care*)

All redundant terms = 0:

x3	x2	x1	x0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0							
1	0	1	1							
1	1	0	0							
1	1	0	1							
1	1	1	0							
1	1	1	1							
1	1	1	1							

$$a = \bar{x}_3 \cdot x_1 + \bar{x}_3 \cdot x_2 \cdot x_0 + x_3 \cdot \bar{x}_2 \cdot \bar{x}_1$$

$$b = \bar{x}_3 \cdot \bar{x}_2 + \bar{x}_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot x_1 \cdot x_0$$

$$c = \bar{x}_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot x_0 + \bar{x}_3 \cdot x_2$$

$$d = \bar{x}_2 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot \bar{x}_2 \cdot x_1 + \bar{x}_3 \cdot x_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_1 \cdot x_0$$

$$e = \bar{x}_2 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot x_1 \cdot \bar{x}_0$$

$$f = \bar{x}_3 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_0 + x_3 \cdot \bar{x}_2 \cdot \bar{x}_1$$

$$g = \bar{x}_3 \cdot \bar{x}_2 \cdot x_1 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_0 + x_3 \cdot \bar{x}_2 \cdot \bar{x}_1$$

1. Redundant terms (*don't care*)

x3	x2	x1	x0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0							
1	0	1	1							
1	1	0	0							
1	1	0	1							
1	1	1	0							
1	1	1	1							
1	1	1	1							
1	1	1	1							

$$b = \bar{x}_3 \cdot \bar{x}_2 + \bar{x}_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot x_1 \cdot x_0$$

x3	x2	x1	x0	b	c
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	0
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	1

$$b = \bar{x}_2 + \bar{x}_1 \cdot \bar{x}_0 + x_1 \cdot x_0$$

1. Redundant terms (*don't care*)

x3	x2	x1	x0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0							
1	0	1	1							
1	1	0	0							
1	1	0	1							
1	1	1	0							
1	1	1	1							
1	1	1	0							
1	1	1	1							

$$c = \bar{x}_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot x_0 + \bar{x}_3 \cdot x_2$$

x3	x2	x1	x0	b	c
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	1	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	0
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	1

$$c = \bar{x}_1 + x_0 + x_2$$

1. Redundant terms (*don't care*)

$$a = \bar{x}_3 \cdot x_1 + \bar{x}_3 \cdot x_2 \cdot x_0 + x_3 \cdot \bar{x}_2 \cdot \bar{x}_1$$

$$b = \bar{x}_3 \cdot \bar{x}_2 + \bar{x}_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot x_1 \cdot x_0$$

$$c = \bar{x}_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot x_0 + \bar{x}_3 \cdot x_2$$

$$d = \bar{x}_2 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot \bar{x}_2 \cdot x_1 + \bar{x}_3 \cdot x_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_1 \cdot x_0$$

$$e = \bar{x}_2 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot x_1 \cdot \bar{x}_0$$

$$f = \bar{x}_3 \cdot \bar{x}_1 \cdot \bar{x}_0 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_0 + x_3 \cdot \bar{x}_2 \cdot \bar{x}_1$$

$$g = \bar{x}_3 \cdot \bar{x}_2 \cdot x_1 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_1 + \bar{x}_3 \cdot x_2 \cdot \bar{x}_0 + x_3 \cdot \bar{x}_2 \cdot \bar{x}_1$$

$$a = x_1 + x_2 \cdot x_0 + x_3$$

$$b = \bar{x}_2 + \bar{x}_1 \cdot \bar{x}_0 + x_1 \cdot x_0$$

$$c = \bar{x}_1 + x_0 + x_2$$

$$d = \bar{x}_2 \cdot \bar{x}_0 + \bar{x}_2 \cdot x_1 + x_1 \cdot \bar{x}_0 + x_2 \cdot \bar{x}_1 \cdot x_0$$

$$e = \bar{x}_2 \cdot \bar{x}_0 + x_1 \cdot \bar{x}_0$$

$$f = \bar{x}_1 \cdot \bar{x}_0 + x_2 \cdot \bar{x}_1 + x_2 \cdot \bar{x}_0 + x_3$$

$$g = \bar{x}_2 \cdot \bar{x}_0 + x_2 \cdot \bar{x}_1 + x_1 \cdot \bar{x}_0 + x_3$$

35	total	26
24	AND	15
7	OR	7
4	INV	26

2. Synthesis tools

Software tools that optimize switching function representations from

- a logic expression,
- a table,

and generate the corresponding circuit.



Two basic concepts:

- CUBE REPRESENTATION,
- ADJACENCY.

2. Synthesis tools

  1) Cubes and cube representation.

- The set of n -component binary vectors $B_2^n = \{(x_{n-1}, x_{n-2}, \dots, x_1, x_0) \in \{0, 1\}^n\}$ can be considered as a **cube of dimension n** .
- A subset of B_2^n defined by giving a constant value (0 or 1) to m coordinates of $(x_{n-1}, x_{n-2}, \dots, x_1, x_0)$ is a **cube of dimension $n-m$** .



2. Synthesis tools

Assume that $n = 4$ and consider a function $f(x_3, x_2, x_1, x_0) = x_2 \cdot \bar{x}_0$:

$$f = 1 \text{ iff } (x_3, x_2, x_1, x_0) \in \{(x_3, x_2, x_1, x_0) \in \{0, 1\}^4, x_2 = 1, x_0 = 0\},$$

that is a cube of dimension $n-2$.

Thus, a **cube** is a set of points of B_2^n where a product of literals = 1.

2. Synthesis tools

Cube representation:

Define a variable order, for example $n-1, n-2, \dots, 1, 0$; then a cube is represented by a sequence of n characters belonging to $\{0, 1, x\}$.

Examples ($n = 4$):

1x01 represents $\{(x_3, x_2, x_1, x_0) \in \{0, 1\}^4, x_3 = 1, x_1 = 0, x_0 = 1\}$; corresponding product: $x_3 \cdot \bar{x}_1 \cdot x_0$.

x1x0 represents $\{(x_3, x_2, x_1, x_0) \in \{0, 1\}^4, x_2 = 1, x_0 = 0\}$; corresponding product: $x_2 \cdot \bar{x}_0$.

1: corresponding variable present under normal form,
0: corresponding variable present under inverted form,
x: corresponding variable missing.

(quiz)

Consider the set of 5-variable switching functions $f(e, d, c, b, a)$. Variable order: e, d, c, b, a .
What cube is represented by $1x01x$?

1. $a.\bar{c}.d$
2. $\bar{a}.c.\bar{d}$
3. $b.e$
4. $e.\bar{c}.b$
5. $\bar{e}.c.\bar{b}$

2. Synthesis tools

2) Adjacency

Consider two cubes ($n = 4$) **1x11** and **1x01**. Assume that the corresponding products

$$x_3 \cdot x_1 \cdot x_0 \text{ and } x_3 \cdot \bar{x}_1 \cdot x_0$$

belong to the representation of some function f :

$$f = x_3 \cdot x_1 \cdot x_0 + x_3 \cdot \bar{x}_1 \cdot x_0 + \dots$$

As they differ in only one variable (x_1 and \bar{x}_1) the representation of f can be simplified:

$$f = x_3 \cdot x_0 + \dots$$

In terms of cubes: $0x11 \cup 0x01 = 0xx1$.

$0x11$ and $0x01$ are **adjacent cubes**.

2. Synthesis tools

EXAMPLE: $f(a,b,c,d)$ defined by a list of cubes

0010, 0011, 0101, 0110, 0111, 1000

(actually a list of minterms of f)

$$0010 \cup 0011 = 001x,$$

$$0110 \cup 0111 = 011x,$$

$$0101 \cup 0111 = 01x1,$$

$$001x \cup 011x = 0x1x.$$

Thus

$$0010 \cup 0011 \cup 0101 \cup 0110 \cup 0111 \cup 1000 = 0x1x \cup 01x1 \cup 1000,$$

$$f = \bar{a} \cdot c + \bar{a} \cdot b \cdot d + a \cdot \bar{b} \cdot \bar{c} \cdot \bar{d}$$

(quiz)

The following set of cubes

$\{0x111, 0x011, 11100, 11101, 11110, 11111\}$

is equivalent to ...

1. $1x111, 111xx, 01011$
2. $111xx$
3. $00x11, 111xx$
4. $0xx11, 111xx$

2. Synthesis tools

LogiSim, Combinational Analysis:

3.1

2. Synthesis tools

x3	x2	x1	x0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0							
1	0	1	1							
1	1	0	0							
1	1	0	1							
1	1	1	0							
1	1	1	1							
1	1	1	1							

$$b = \bar{x}_2 + \bar{x}_1 \cdot \bar{x}_0 + x_1 \cdot x_0$$

$$c = \bar{x}_1 + x_0 + x_2$$

3.1

$$f = \overline{a} + \overline{b} \cdot \overline{c} + a \cdot b \cdot c + \overline{a} \cdot d \cdot e$$

$$f = !a + !b \& !c + a \& b \& c + !a \& d \& e$$

SUMMARY

- Redundant terms and corresponding optimization problem.
- Relation between cubes and products of literals.
- Tools that minimize Boolean expressions and that optimize circuits.

3.2 Propagation time

Jean-Pierre Deschamps

University Rovira i Virgili, Tarragona, Spain



1. Propagation time

Logic gates are electronic components characterized by their propagation time, from their inputs to their outputs.

1. Propagation time



Logic gates are electronic components characterized by their propagation time, from their inputs to their outputs.

a) Logic gate:

  

1. Propagation time

b) Combinational circuit (“worst case”)

  

$$a = 0, b = x, c = 1 \rightarrow 0, d = 1, e = 0$$

1. Propagation time

To different implementations of the same function correspond different delays. Example:


$$f = [(a+b).(c+d).e] + [(k+g).(h+i).j]$$

$$f = e.a.c + e.a.d + e.b.c + e.b.d + j.k.h + j.k.i + j.g.h + j.g.i$$

 
1. Propagation time

To different implementations of the same function correspond different delays. Example:

$$f = [(a+b).(c+d).e] + [(k+g).(h+i).j]$$



 
$$f = e.a.c + e.a.d + e.b.c + e.b.d + j.k.h + j.k.i + j.g.h + j.g.i$$



 1. Propagation time

To different implementations of the same function correspond different delays. Example:


$$f = [(a+b).(c+d).e] + [(k+g).(h+i).j]$$



gates = 7
 $t_p \approx 3 \cdot \tau$


SPEED vs. COST BALANCE
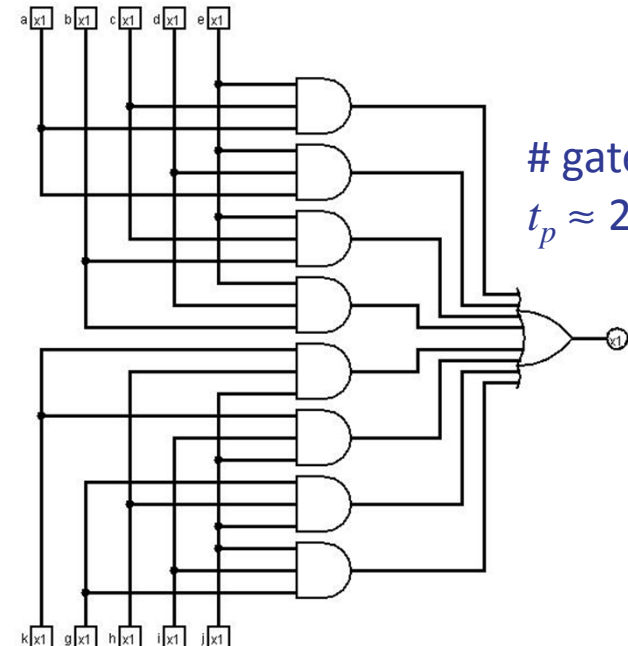
$$f = e.a.c + e.a.d + e.b.c + e.b.d + j.k.h + j.k.i + j.g.h + j.g.i$$




gates = 9
 $t_p \approx 2 \cdot \tau$

2. Example: n -bit comparator

 

```
if X > Y then G <= 1;  
  elsif X < Y then L <= 1;  
    else E <= 1;  
  end if;  
end if;
```


2. Example: n -bit comparator

 

	$n-1$	$n-2$	$n-3$	$n-4$	1	0
X:	1	0	1	1	0	...	0	0
Y:	1	0	1	0	1	...	1	0

$G_n=0$								
$L_n=0$								




2. Example: n -bit comparator

 

	$n-1$	$n-2$	$n-3$	$n-4$	1	0
X:	1	0	1	1	0	...	0	0
Y:	1	0	1	0	1	...	1	0


$G_n=0$	0	0	0	1	1		1	1
$L_n=0$	0	0	0	0	0		0	0

2. Example: n -bit comparator

   


(Exercise)

Implement a 1-bit comparator

 

(Solution)


Implement a 1-bit comparator

 

G_{i+1}	L_{i+1}	x_i	y_i	G_i	L_i
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	x	x		
1	0	x	x		
1	1	x	x		

(Solution)

Implement a 1-bit comparator

 


G_{i+1}	L_{i+1}	x_i	y_i	G_i	L_i
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	x	x	0	1
1	0	x	x	1	0
1	1	x	x	x	x

$$G_i = \bar{L}_{i+1} \cdot x_i \cdot \bar{y}_i + G_{i+1}$$

$$L_i = \bar{G}_{i+1} \cdot \bar{x}_i \cdot y_i + L_{i+1}$$

2.1. Component: 1-bit comparator

 


$$G_i = \bar{L}_{i+1} \cdot x_i \cdot \bar{y}_i + G_{i+1}$$

$$L_i = \bar{G}_{i+1} \cdot \bar{x}_i \cdot y_i + L_{i+1}$$


Every 1-bit comparator: $3 \cdot \tau$
8 gates.

 n -bit comparator: $(3 \cdot n + 1) \cdot \tau$
 $(8 \cdot n + 1)$ gates



(Exercise)


Design a 2-bit comparator

 

(Solution)

Design a 2-bit comparator


G_{i+1}	L_{i+1}	x_i	x_{i-1}	y_i	y_{i-1}	G_{i-1}	L_{i-1}
0	0	0	0	0	0		
0	0	0	0	1	x		
0	0	0	0	x	1		
0	0	0	1	0	0		
0	0	0	1	0	1		
0	0	0	1	1	x		
0	0	1	0	0	x		
0	0	1	0	1	0		
0	0	1	0	1	1		
0	0	1	1	0	x		
0	0	1	1	x	0		
0	0	1	1	1	1		
0	1	x	x	x	x		
1	0	x	x	x	x		
1	1	x	x	x	x	x	x

 

(Solution)

Design a 2-bit comparator


G_{i+1}	L_{i+1}	x_i	x_{i-1}	y_i	y_{i-1}	G_{i-1}	L_{i-1}
0	0	0	0	0	0	0	0
0	0	0	0	1	x	0	1
0	0	0	0	x	1	0	1
0	0	0	1	0	0	1	0
0	0	0	1	0	1	0	0
0	0	0	1	1	x	0	1
0	0	1	0	0	x	1	0
0	0	1	0	1	0	0	0
0	0	1	0	1	1	0	1
0	0	1	1	0	x	1	0
0	0	1	1	x	0	1	0
0	0	1	1	1	1	0	0
0	1	x	x	x	x	0	1
1	0	x	x	x	x	1	0
1	1	x	x	x	x	x	x

 

$$G_{i-1} = \bar{L}_{i+1} \cdot x_{i-1} \cdot \bar{y}_i \cdot \bar{y}_{i-1} + \bar{L}_{i+1} \cdot x_i \cdot \bar{y}_i + \bar{L}_{i+1} \cdot x_i \cdot x_{i-1} \cdot \bar{y}_{i-1} + G_{i+1}$$


$$L_{i-1} = \bar{G}_{i+1} \cdot \bar{x}_i \cdot \bar{x}_{i-1} \cdot y_{i-1} + \bar{G}_{i+1} \cdot \bar{x}_i \cdot y_i + \bar{G}_{i+1} \cdot \bar{x}_{i-1} \cdot y_i \cdot y_{i-1} + L_{i+1}$$

2.2. Component: 2-bit comparator

 

Every 2-bit comparator: $3 \cdot \tau$
14 gates.

 n -bit comparator: $(1.5 \cdot n + 1) \cdot \tau$
 $(7 \cdot n + 1)$ gates



2.3. n -bit comparator

	1bit comparator	2-bit comparator
#gates	8	14
t_p	3	3

	n -bit comparator	
	C 1bit	C 2 bits
#gates	$8 \cdot n + 1$	$7 \cdot n + 1$
t_p	$(3 \cdot n + 1)\tau$	$(1.5 \cdot n + 1)\tau$

	32-bit comparator	
	C 1bit	C 2 bits
#gates	257	225
t_p	97τ	49τ

SUMMARY

- Propagation time.
- Speed vs. Cost.
- n -bit comparator: two implementations have been compared.

3.3 OTHER LOGIC BLOCKS


Jean-Pierre Deschamps

University Rovira i Virgili, Tarragona, Spain

1. Multiplexers.

Mainly used to implement **controllable connections**.


MUX2-1
(2-to-1 multiplexer)

 

<i>control</i>	<i>y</i>
0	x_0
1	x_1

1. Multiplexers.

typical application:

 


control = 1: *circuit_C* input connected to *circuit_A* output;

control = 0: *circuit_C* input connected to *circuit_B* output.

 1. Multiplexers.

Other multiplexers:


- m -bit 2-to-1 multiplexer:
 m 2-to-1 multiplexers controlled
by the same signal *control*
(x_0, x_1 : m -bit vectors)



1. Multiplexers.

MUX4-1

(4-to-1 multiplexer,
2 control signals)

 


$c_1 c_0$	y
00	x_0
01	x_1
10	x_2
11	x_3

8-to-1 multiplexers with 3 control signals,
16-to-1 multiplexers with 4 control signals,
...
can be defined.

3.3



 
(Exercise)

Design a 2-bit 4-to-1 multiplexer using 1-bit 2-to-1 multiplexers.



(Solution)

 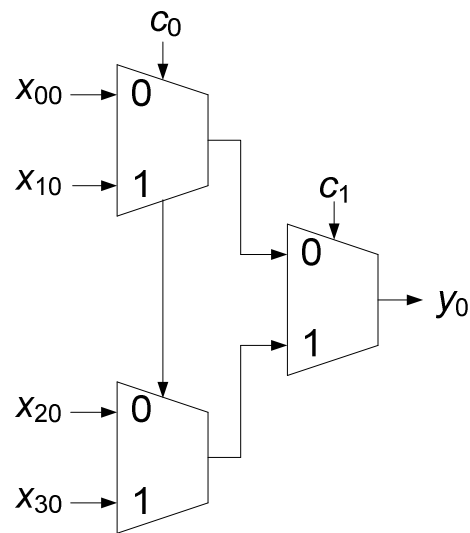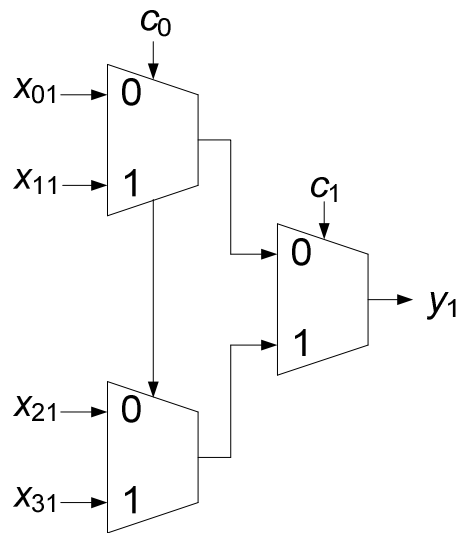Design a 2-bit 4-to-1 multiplexer using 1-bit 2-to-1 multiplexers.



(Quiz)

Mark the correct statements (MUX=multiplexer)



- ☐ 4 1-bit 2-1 MUXs are required to synthesize a 1-bit 4-1 MUX
- ☐ 12 1-bit 2-1 MUXs are required to synthesize a 4-bit 4-1 MUX
- ☐ 7 1-bit 2-1 MUXs are required to synthesize a 1-bit 8-1 MUX
- ☐ 21 1-bit 2-1 MUXs are required to synthesize a 3-bit 8-1 MUX

1. Multiplexers.

Multiplexers can also be used to implement functions defined by tables.



Example:

x_2	x_1	x_0	y_1	y_0
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

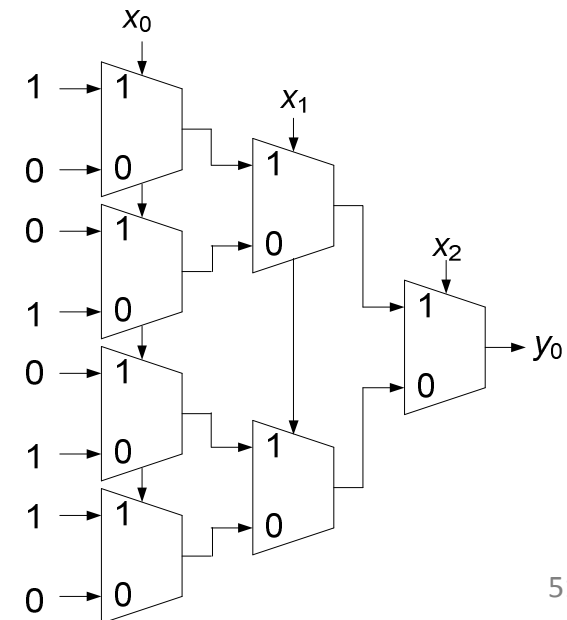 

1. Multiplexers.

Example of (trivial) optimization rules:

 
 


(Exercise)

Optimize the preceding circuit.

3.3

UAB
Universitat Autònoma
de Barcelona

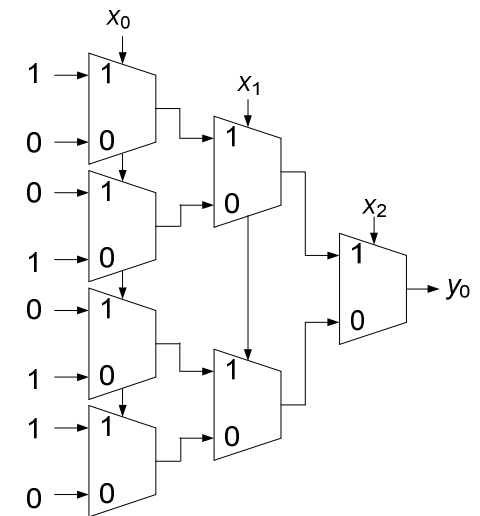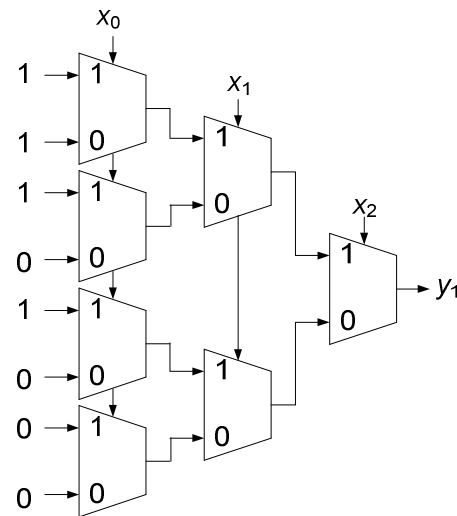


(Solution)

Optimize the preceding circuit.

3.3

UAB
Universitat Autònoma
de Barcelona

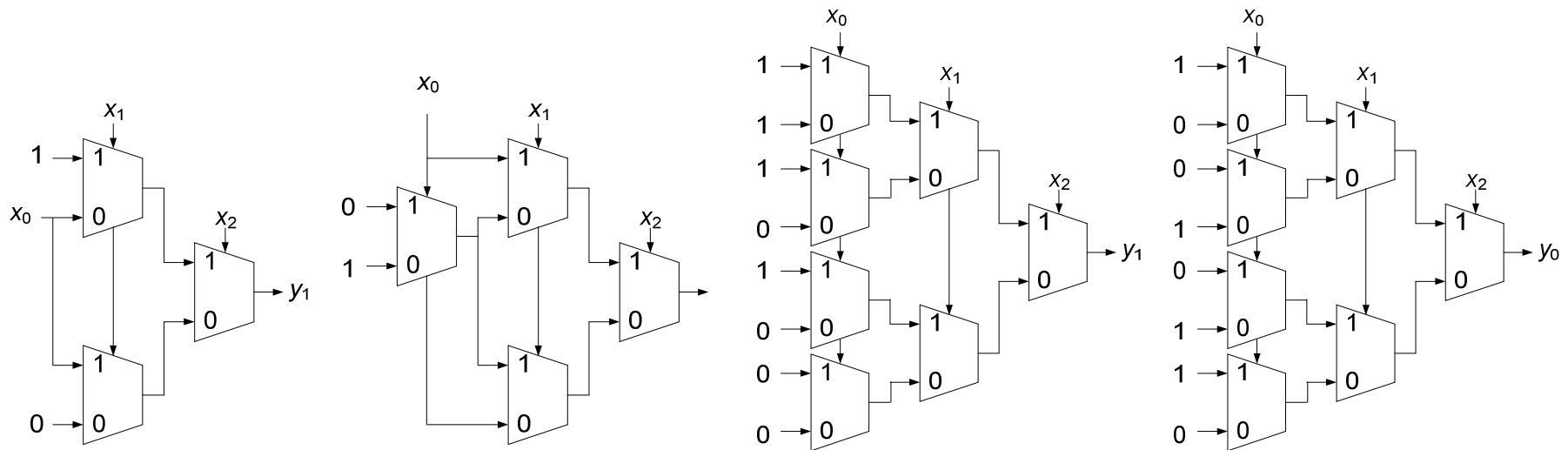

1. Multiplexers.


Comment

A multiplexer-based synthesis method is based on an iterative application of the following simple rule:

$$f(x_0, x_1, \dots) = \bar{x}_0 \cdot f(0, x_1, \dots) + x_0 \cdot f(1, x_1, \dots)$$

Subfunctions $f(0, x_1, \dots)$ and $f(1, x_1, \dots)$ are functions of $n-1$ variables.

 Iteratively application => constant values, simple variables, or already available subfunctions.



2. Multiplexers and memory blocks.

Read Only Memory (ROM) blocks have been used to implement functions defined by a table.


More generally consider the use of

small ROM (**LUT = Look Up Tables**) + multiplexers.

 Example: assume that 6-input LUT's are available. Iteratively apply

$$f(x_0, x_1, \dots) = \bar{x}_0 \cdot f(0, x_1, \dots) + x_0 \cdot f(1, x_1, \dots)$$


until all obtained subfunctions are functions of at most 6 variables.



2. Multiplexers and memory blocks.

3.3


Example: 8-variable function

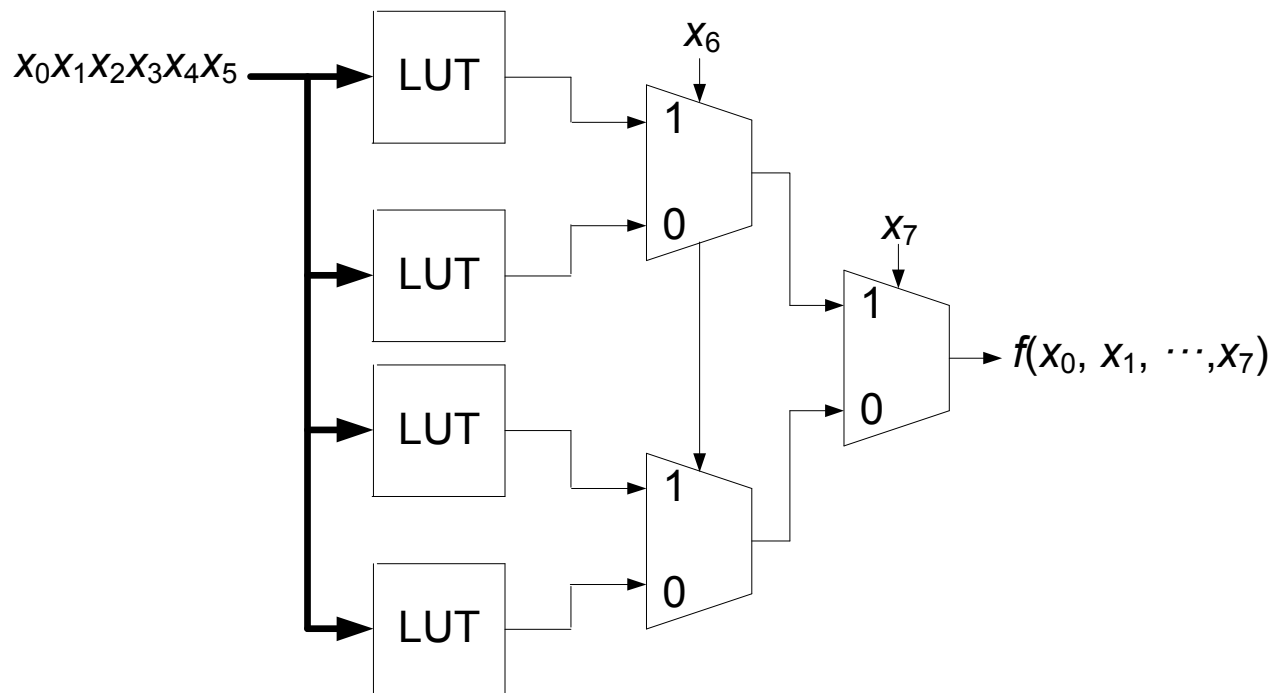

2. Multiplexers and memory blocks.

3.3

Example: 8-variable function (with LUTs)

 

2. Multiplexers and memory blocks.

Comment


The preceding example is based on an iterative application of the following simple rule:

$$f(x_0, x_1, \dots) = \bar{x}_0 \cdot \bar{x}_1 \cdot f(0, 0, x_2, \dots) + x_0 \cdot \bar{x}_1 \cdot f(1, 0, x_2, \dots) + \bar{x}_0 \cdot x_1 \cdot f(0, 1, x_2, \dots) + x_0 \cdot x_1 \cdot f(1, 1, x_2, \dots).$$

Subfunctions $f(0, 0, x_2, \dots)$, $f(0, 1, x_2, \dots)$, $f(1, 0, x_2, \dots)$ and $f(1, 1, x_2, \dots)$ are functions of $n-2$ variables.

Iteratively application => constant values, simple variables, or already available subfunctions.

3.3

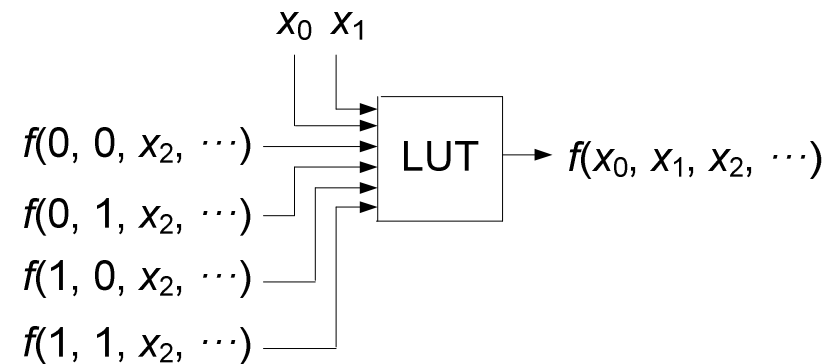


(Quiz)

How many 6-input LUTs are necessary to synthesize any 10-variable switching function?

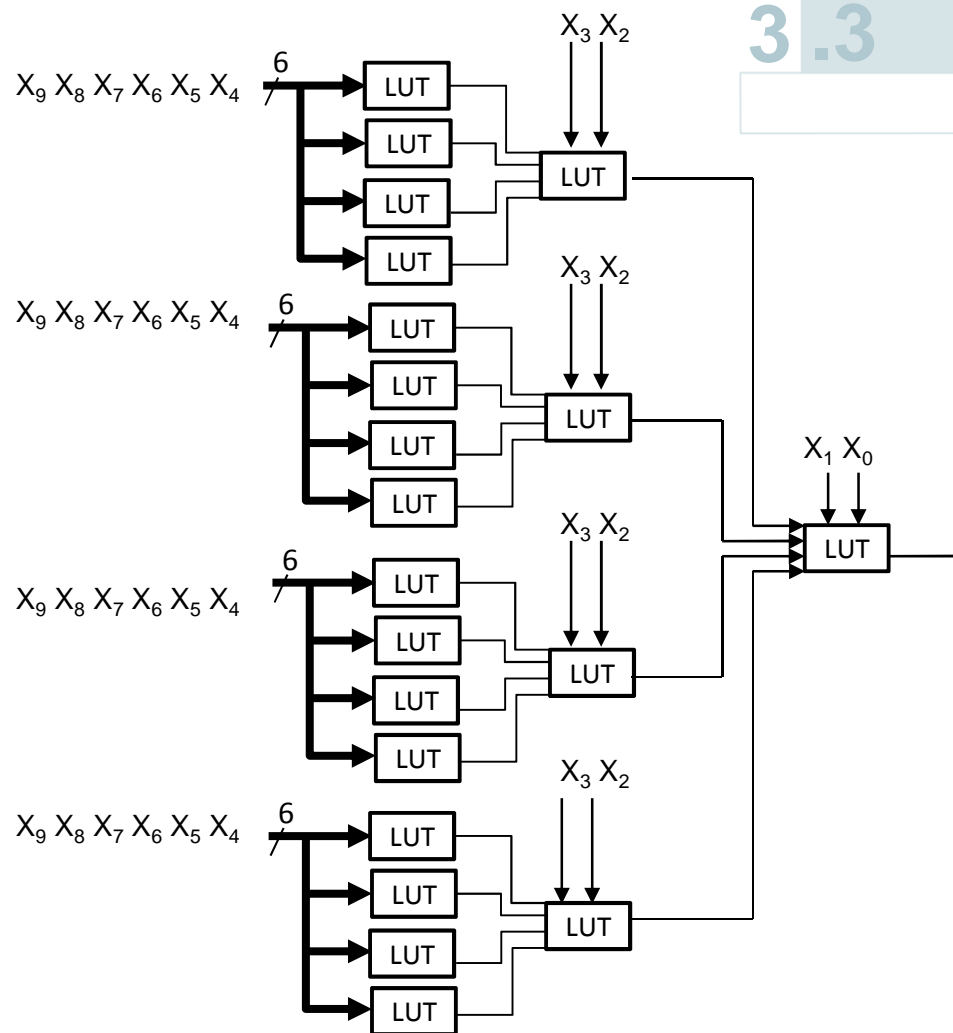1. 21
2. 32
3. 64
4. 128

Circuit implementing the 10 variables switching function

(this slide is not included in the video)



3.3

3. Planes.


(n, p) AND-plane: implements
 p n -variable functions y_j ;

each y_j is a product of literals:

$y_j = w_{j,0}w_{j,1} \cdots w_{j,n-1}$ where
 $w_{j,i} \in \{1, x_i, \bar{x}_i\}$.

According to the technology, functions y_j can
be

 - predefined
- defined by the user ([field programmable](#)).



3. Planes.

(p, s) OR-plane: implements
 s p -variable functions z_j ;


each z_j is a Boolean sum of variables :

$$z_j = w_{j,0} \vee w_{j,1} \vee \dots \vee w_{j,p-1}$$

where $w_{j,i} \in \{0, y_i\}$.

Functions z_j can be

 - predefined
- defined by the user (**field programmable**).




3.3

3. Planes.

Any set of s Boolean functions that can be expressed as Boolean sums of at most p products of at most n literals can be implemented by a circuit made up of

- an (n, p) AND plane,
- a (p, s) OR plane.

 Different names according to the technology and/or the manufacturer ([PAL](#), [PLA](#), [PLD](#), ...).




4. Address decoders and 3-state buffers.

n-to- 2^n address decoder:

- n inputs $x_{n-1} x_{n-2} \cdots x_0$,
- $m = 2^n$ outputs $y_0 y_1 \cdots y_{m-1}$,
- $y_i = 1$ iff $x_{n-1} \cdot 2^{n-1} + x_{n-2} \cdot 2^{n-2} + \cdots + x_1 \cdot 2 + x_0 = i$.

Example: 2-to-4 address decoder

 

x_1	x_0	y_0	y_1	y_2	y_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

4. Address decoders and 3-state buffers.

Comments


- An address decoder implements the same function as an $(n, 2^n)$ AND plane that generates the 2^n n -variable minterms

$$m_j = w_{j,0} w_{j,1} \cdots w_{j,n-1}$$

where $w_{j,i} \in \{x_i, \bar{x}_i\}$.

- Address decoder + $(2^n, s)$ OR plane: same function as a ROM storing 2^n s -bit word.


Example: 2-variable functions.

 

4. Address decoders and 3-state buffers.

Address decoders can be used to control 3-state buffers.

 Example (y_0, y_1, y_2, y_3 and z are 4-bit vectors):
equivalent to a 4-bit MUX4-1



4. Address decoders and 3-state buffers.

When $x_1 x_0 =$


00: $circuit_E \leftarrow circuit_A;$

01: $circuit_E \leftarrow circuit_B;$


00: $circuit_E \leftarrow circuit_C;$

00: $circuit_E \leftarrow circuit_D;$

= example of **BUS**

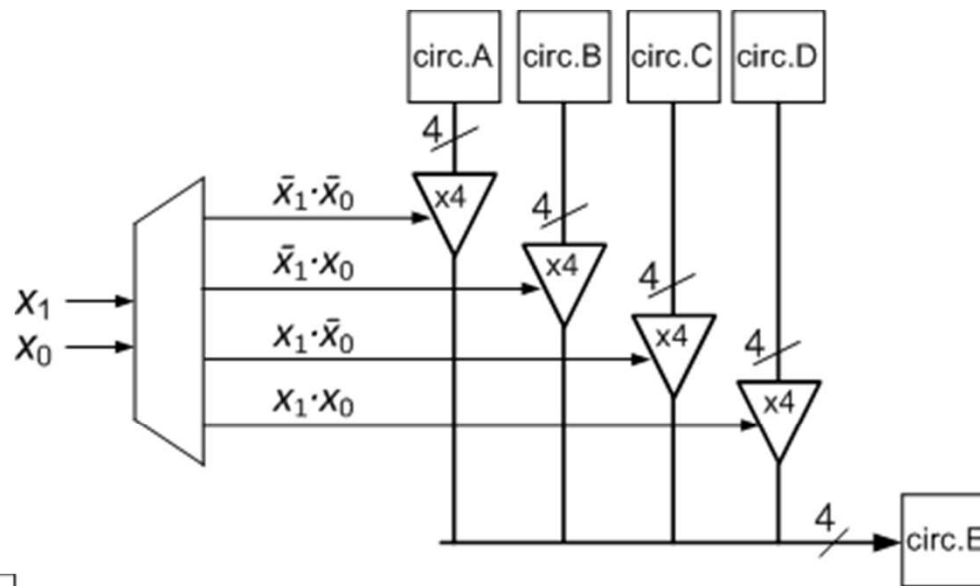

Symbol:

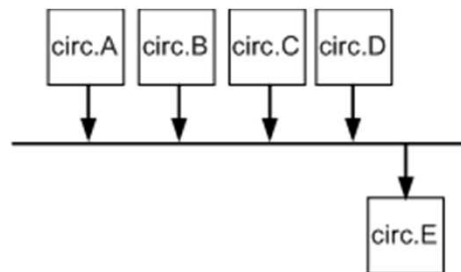

SUMMARY

- Multiplexers implement controllable connections.
- Multiplexers can also be used to implement Boolean functions.
- Small memory blocks (Look Up Tables) are used to implement Boolean functions.
- Predefined or field programmable planes are used to implement Boolean functions.
- Address decoders and 3-state buffers implement buses.

3.4 PROGRAMMING LANGUAGE STRUCTURES

Jean-Pierre Deschamps

University Rovira i Virgili, Tarragona, Spain


Some classical programming language instructions have a straightforward translation in terms of digital components. Examples:

1. If ... then ... else ...
2. Case ... is ...
3. For ... loop ...
4. Procedure call

1. If ... then ... else ...

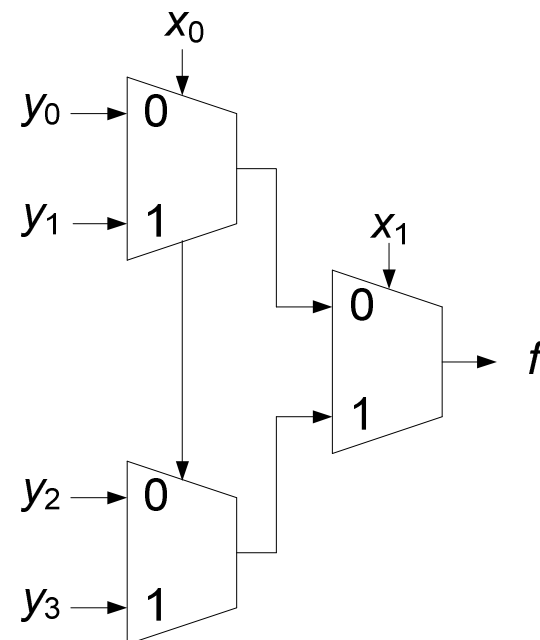Example: a binary decision algorithm.


```
if  $x_1 = 0$  then  
  if  $x_0 = 0$  then  $f \leq y_0$ ;  
  else  $f \leq y_1$ ;  
  end if;  
else  
  if  $x_0 = 0$  then  $f \leq y_2$ ;  
  else  $f \leq y_3$ ;  
  end if;  
end if;
```



2. Case ... is ...

 Example: program equivalent to the preceding binary decision algorithm.

```
case x is  
  when "00" => f <=  $y_0$ ;  
  when "01" => f <=  $y_1$ ;  
  when "10" => f <=  $y_2$ ;  
  when "11" => f <=  $y_3$ ;  
end case;
```



3. For ... loop ...

3.4


Loops are associated with iterative structures.

Example: addition algorithm that computes $z = x + y$
(x and y : 4-digit decimal numbers,
 z : 5-digit decimal number)

```
cy(0) <= 0;  
for i in 0 to 3 loop  
  s(i) <= x(i) + y(i) + cy(i);  
  if s(i) > 9 then z(i) <= s(i) - 10; cy(i+1) <= 1;  
  else z(i) <= s(i); cy(i+1) <= 0;  
  end if;  
end loop;  
z(4) <= cy(4);
```

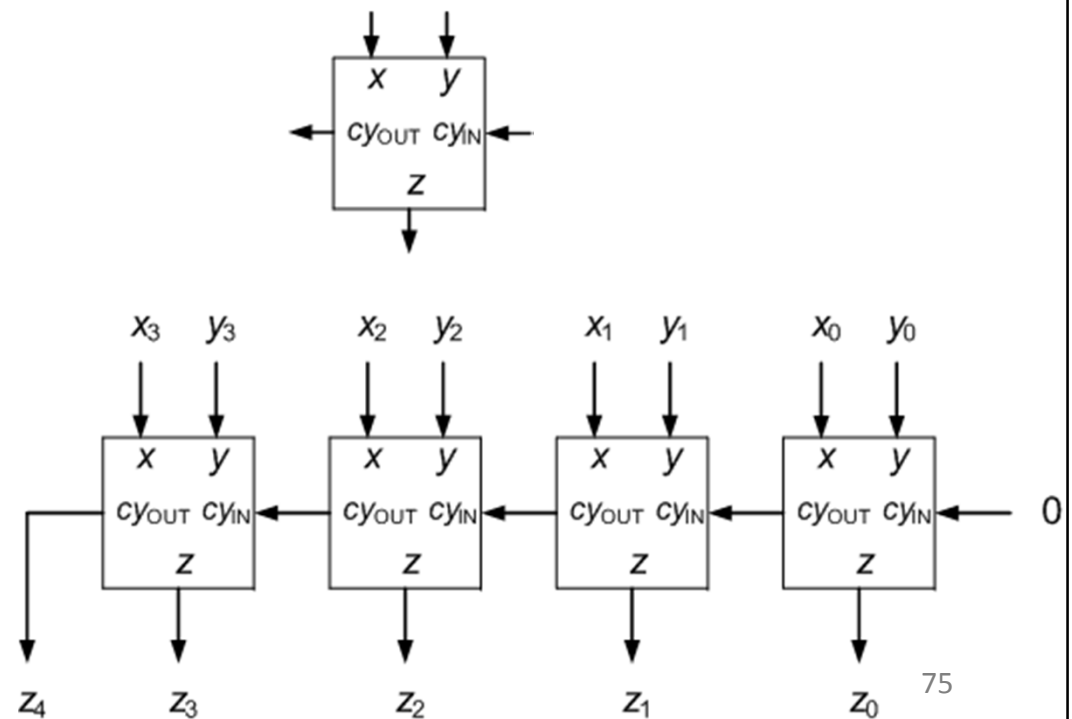3. For ... loop ...

```
cy(0) <= 0;  
for i in 0 to 3 loop  
----- loop body -----  
    s(i) <= x(i) + y(i) + cy(i);  
    if s(i) > 9 then z(i) <= s(i) - 10; cy(i+1) <= 1;  
    else z(i) <= s(i); cy(i+1) <= 0;  
    end if;  
-----  
end loop;  
z(4) <= cy(4);
```



3. For ... loop ...

3.4

Comments.

- Other (sequential) implementations will be seen later on.
- Not any loop can be implemented in this way.

Example: "while *condition* loop *operation*".

If the maximum number of times that *condition* holds true

- ✓ is unknown,
- ✓ is a too large number,

a sequential implementation must be considered.

4. Procedure call

Example: assume that a procedure $\text{MAC}(w, x, y, z)$ (multiply and accumulate) has been defined; it executes

$$z = w + x \cdot y.$$

The following algorithm computes

$$z = x_1 \cdot y_1 + x_2 \cdot y_2 + \cdots + x_8 \cdot y_8:$$

```
w(1) <= 0;  
for i in 1 to 8 loop  
  MAC(w(i), x(i), y(i), w(i+1));  
end loop;  
z <= w(9);
```

4. Procedure call


```

w(1) <= 0;
for i in 1 to 8 loop
  MAC(w(i), x(i), y(i), w(i+1));
end loop;
z <= w(9);
  
```

Conclusion:

- for ... loop => iterative structure;
- MAC calls => blocks to be defined.

 Procedure calls are associated with hierarchical descriptions.



5. COMMENTS

Conclusion: some classical programming language instructions have a straightforward translation in terms of digital components =>

- define programming languages to specify digital systems (VHDL, Verilog, C/C++); (the so-called **Hardware Description Languages**)
- develop synthesis tools (software) to translate programs to circuits.

SUMMARY

- Binary decision algorithm can be implemented with multiplexers.
- Case constructs can also been implemented by multiplexers.
- Loops correspond to iterative structures.
- Procedure calls correspond to hierarchical descriptions
- A conclusion about Hardware Description Languages and Synthesis tools.